 


# EE1193

## Introduction to Hardware Description Language

### Pseudo Code and Block Diagram of Pipeline Processor



### *Schematic Diagram for Functioning of a Pipeline Processor*

## **Pseudo Code**

```
module Adder (output wire cout, output wire [7:0] s, input wire [7:0] x,y, input wire cin);  
//This module adds 2 '8' bit numbers
```

```
wire sel[7:0];  
wire c[8:0];  
assign c[0] = cin;  
  
    genvar i;  
    generate  
        for(i = 0; i < 8; i = i + 1)  
            begin  
                Xor s0(sel[i],x[i],y[i]);  
                Mux m0(c[i+1],y[i],c[i],sel[i]);    //Using MUX to calculate  
next carry states  
                Xor z0(s[i],sel[i],c[i]);    //Final Sum  
            end  
    endgenerate  
  
assign cout = c[8];  
  
endmodule
```

```
module proc(output wire [7:0] y, input wire [31:0] x,input wire clk);  
reg sel;  
wire t,cin,s;    //Declaring all wires and registers  
reg [7:0] a,b,z,z1,c1,i1,c,o;  
wire [7:0] p;  
reg [7:0] storage [255:0];    //Memory Element for storage of the Data  
  
integer k;  
// Decoder stage  
assign s = x[31];    // Taking a selector for the mux in the executor stage  
  
assign cin = 0;
```

```
//Execution Stage  
Adder j1(t,p,a,b,cin);
```

```
always @(sel) //Changes happening at change of selector  
begin  
    if (sel == 0) //Operation regarding value of sel  
        begin  
            z = a & b; //"AND" Operation of 2 bytes  
        end  
  
    else  
        begin  
            z = p; //Adding 2 bytes  
        end  
  
end
```

```
always @(posedge clk)//(Pipelining) pushing the values to registers after each clock cycles  
begin  
    sel <= s; //From 's' the data goes to sel after one clock cycle  
    a <= x[15:8]; //From input the data goes to a after one clock cycle  
    b <= x[7:0]; //Similar to a  
    z1 <= z; //z is the output from the executor stage, data being sent to register  
    o<=z1;  
    c1 <= x[23:16]; // X[23:16] is the address where the data has to be stored  
    k <= c1; //Converting Binary output to an integer  
end
```

```
// Write back Stage
```

```
always@(*)  
begin  
    storage[k] = o; //Storing output in Memory  
end
```

```
assign y = storage[k]; //Assigning data in memory  
to output wire to display
```

```
Endmodule
```

```

module test; //Test Bench
localparam width = 32;
wire [7:0] y; //Output
reg [width-1:0] x; //Input
reg clk; //Clock
reg [7:0] store [255:0]; //Memory

initial
begin
    clk = 1;

end

always #5 clk = ~clk; //Generating a clock of period 5
initial begin //Inputs ; They get assigned during rising edge of clock

    x = 98765483280;
    @(posedge clk)
#10
    x = 1234567890;
    @(posedge clk)
#10
    x = 32'b11000001111001010111001101100001;
    @(posedge clk)
#10
    x = 98765483280;
    @(posedge clk);
    @(posedge clk);
    $finish;
end


proc r1(y,x,clk); //Calling Module
initial begin
    $monitor("Output: %b Input: %b",y, x);
//Monitoring the Output

end

initial begin
    $dumpfile("Project.vcd");
    //Generating .vcd File
    $dumpvars;
end
endmodule

```

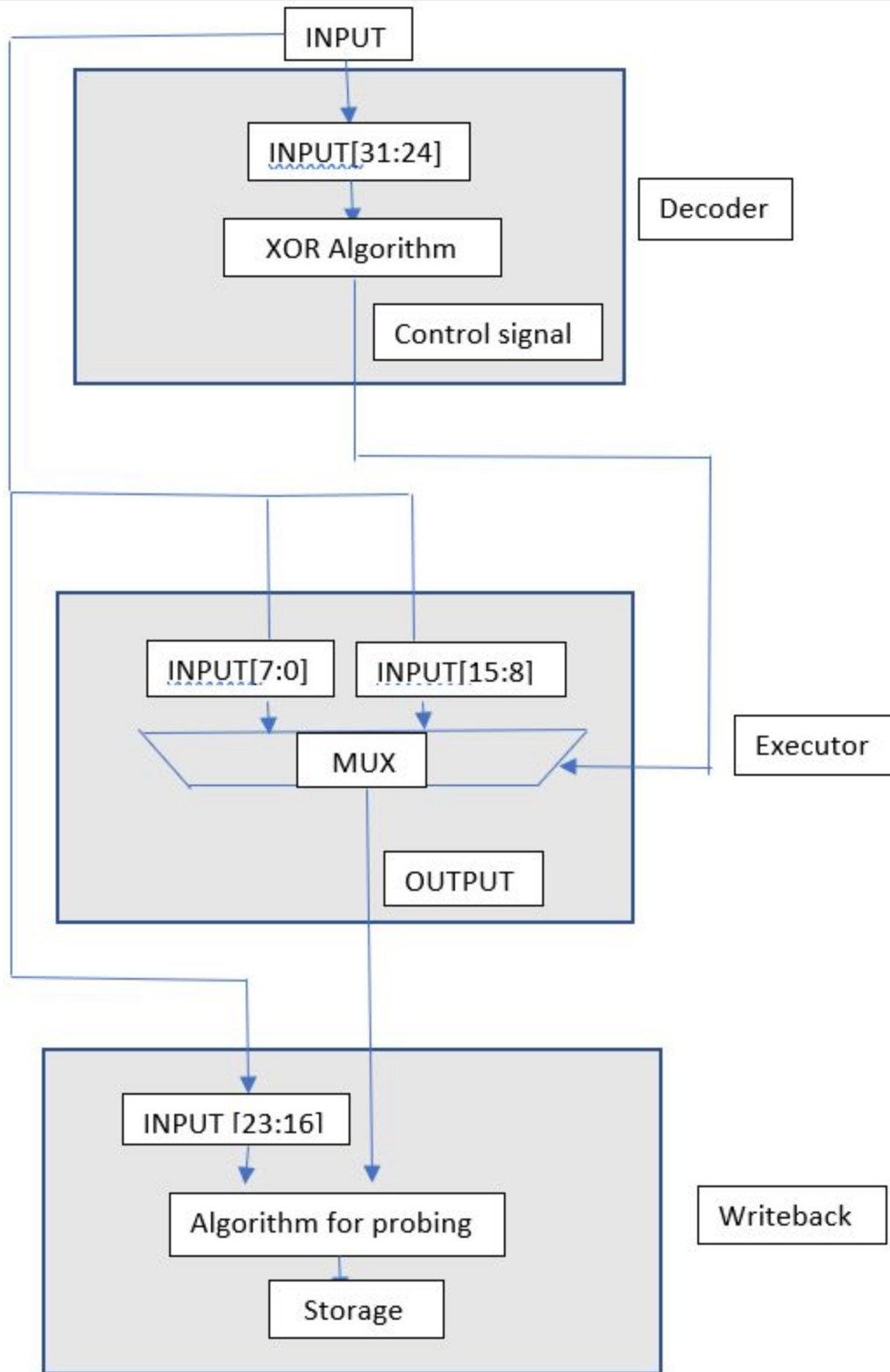**Block Diagram For Execution of Pipeline Processor**



### **INSTRUCTIONS FOR EXECUTING CODE**

The module takes a input executes it and produces output. The output is being stored in a memory.

So, we have to give one input at each clock cycle and output generated is printed .

Go to the directory in which code is present.

Open terminal in that directory,

type: iverilog -o sim fif\_tb.v proc.v

then for simulation type : vvp sim.

**Submitted by:**

***Akash Tadvai - ES18BTECH11019***

***Vamshi T - ES18BTECH11021***